

# Finite State Machine Styles


CS152A – 2015 Fall

# What's in an FSM?

- These slides assume that you already know what an FSM is in the general sense.
- In digital design, an FSM has 3 components:
  - Inputs, can be events (pulses) or states (levels)
  - Outputs, can be events (pulses) or states (levels)
  - State transition logic that depend on only inputs and current states

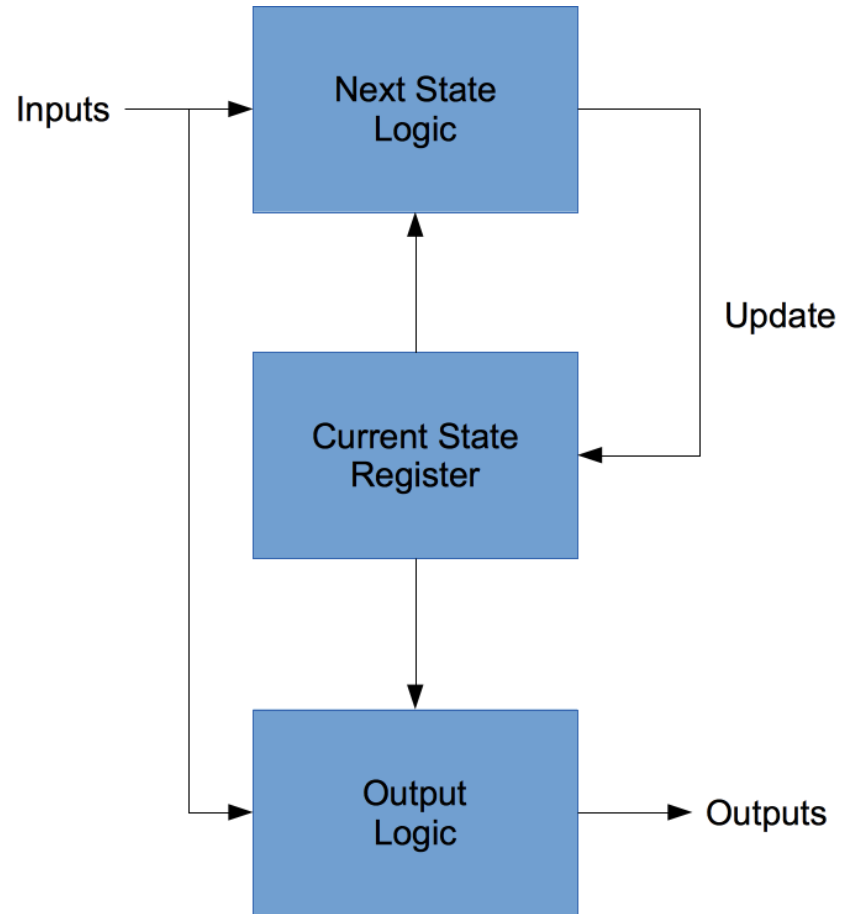
# Mealy Machine

- In the conventional sense, a Mealy machine is a state machine whose outputs depend on both the current state and the input states
- A change in input may be immediately reflected in the output


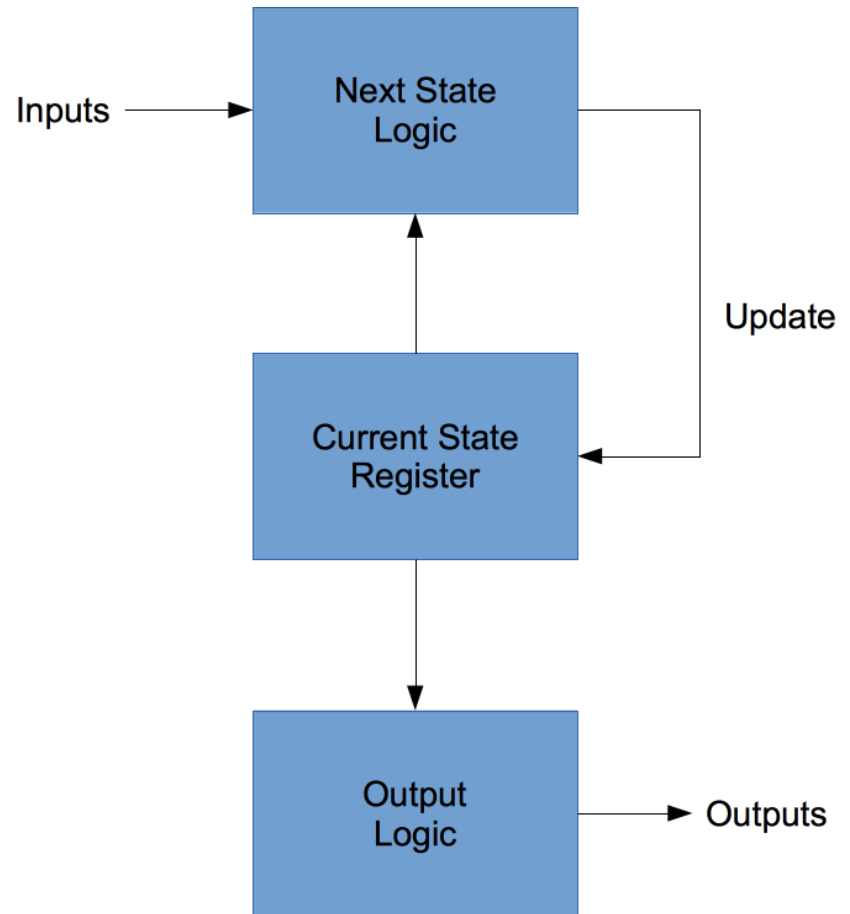
# Moore Machine

- In the conventional sense, a Moore machine is a state machine whose outputs only depend on the current state
- Outputs always change one cycle behind input change



# Mealy vs Moore

- Advantages of Mealy-style machines
  - Low-latency output
  - Fewer states than equivalent Moore-style machines
- Advantages of Moore-style machines
  - More clean separation of inputs and outputs
  - Can guarantee stability of output
  - Better for static timing

# Mealy vs. Moore, cont.


- So when do you use Mealy- or Moore-style FSM?
- Mealy and Moore are mere conceptual boxes that we (engineers) draw on designs
- In reality, few really think about FSMs in terms of Mealy or Moore
- Both will get the job done; in practice, most of our designs are Moore machines

# FSM Design Tips

- Start your FSM design by first drawing the STD (State Transition Diagram) on paper
- Once you are convinced that your STD achieves your design goal, translate it to HDL
- Typical FSM has three conceptual blocks:
  - A combinational block that computes the next state
  - A sequential block that builds the state register
  - A combinational/sequential block that generates the output
- In reality many designers choose to combine these blocks to one or two blocks
 
# Verilog Example

- Design a state machine that recognize the following input sequence: 01110
- Inputs: i\_data
- Output: o\_valid (pattern detected)
- States: idle, 0, 01, 011, 0111, 01110
- Is this a Mealy or Moore machine?





# Part I – declarations

```
output o_valid;  
input i_data;  
input clk;  
input srst;
```

```
parameter stldle = 0;  
parameter st0    = 1;  
parameter st01   = 2;  
parameter st011  = 3;  
parameter st0111 = 4;  
parameter st01110 = 5;
```

```
reg [2:0] cur_state;  
reg [2:0] nxt_state;
```

- Why are the width of cur\_state and nxt\_state 3 bits wide?
- cur\_state is a sequential logic element that stores the current state
- nxt\_state is a combinational variable, not registerd

# Part II – State Register Block

Synchronous reset example:

```
always @ (posedge clk)
  if (srst)
    cur_state <= stidle;
  else
    cur_state <= nxt_state;
```

Asynchronous reset example:

```
always @ (posedge clk or posedge arst)
  if (arst)
    cur_state <= stidle;
  else
    cur_state <= nxt_state;
```

# Part III – Next State Logic

```
always @*  
case (cur_state)  
  stldle : nxt_state = i_data ? stldle : st0;  
  st0    : nxt_state = i_data ? st01 : st0;  
  st01   : nxt_state = i_data ? st011 : stldle;  
  st011  : nxt_state = i_data ? st0111 : stldle;  
  st0111 : nxt_state = i_data ? stldle : st01110;  
  st01110 : nxt_state = i_data ? stldle : st0;  
  default : nxt_state = cur_state;  
endcase
```

Think: what would happen if the default clause was left out?

# Part III – Next State Logic

always @\*

case (cur\_state)

stIdle : nxt\_state = i\_data ? stIdle : st0;

st0 : nxt\_state = i\_data ? st01 : st0;

st01 : nxt\_state = i\_data ? st011 : stIdle;

st011 : nxt\_state = i\_data ? st0111 : stIdle;

st0111 : nxt\_state = i\_data ? stIdle : st01110;

st01110 : nxt\_state = i\_data ? stIdle : st0;

default : nxt\_state = cur\_state;

endcase

Think: what would happen if the default clause was left out?

**Answer: a `nxt_state` latch will be created!**

# Part IV – Output Logic Block

```
assign o_valid = (cur_state==st01110);
```

That's it!

What would a Mealy machine's output look like?

```
assign o_valid = (cur_state==st0111) & ~data_i;
```

# Combining Current and Next State Block

```
always @ (posedge clk)
  if (srst)
    cur_state <= stldle;
  else
    case (cur_state)
      stldle : cur_state <= i_data ? stldle : st0;
      st0    : cur_state <= i_data ? st01  : st0;
      st01   : cur_state <= i_data ? st011 : stldle;
      st011  : cur_state <= i_data ? st0111 : stldle;
      st0111 : cur_state <= i_data ? stldle : st01110;
      st01110 : cur_state <= i_data ? stldle : st0;
    endcase
```

Think: why don't we need the default clause any more?

# Combining Current and Next State Block

```
always @ (posedge clk)
  if (srst)
    cur_state <= stidle;
  else
    case (cur_state)
      stidle : cur_state <= i_data ? stidle : st0;
      st0    : cur_state <= i_data ? st01  : st0;
      st01   : cur_state <= i_data ? st011 : stidle;
      st011  : cur_state <= i_data ? st0111 : stidle;
      st0111 : cur_state <= i_data ? stidle : st01110;
      st01110 : cur_state <= i_data ? stidle : st0;
    endcase
```

Think: why don't we need the default clause any more?

**Answer: cur\_state is already a sequential register**

# State Register Encoding

Suppose the state encoding was the following:

```
parameter stIdle = 4'b0000;  
parameter st0    = 4'b0001;  
parameter st01   = 4'b0010;  
parameter st011  = 4'b0011;  
parameter st0111 = 4'b0100;  
parameter st01110 = 4'b1000;
```

If we assume all other states are illegal states (not possible to obtain), how would this encoding simplify the output logic?

How would this encoding impact the next state logic?



# State Register Encoding

Suppose the state encoding was the following:

```
parameter stIdle = 4'b0000;  
parameter st0    = 4'b0001;  
parameter st01   = 4'b0010;  
parameter st011  = 4'b0011;  
parameter st0111 = 4'b0100;  
parameter st01110 = 4'b1000;
```

If we assume all other states are illegal states (not possible to obtain), how would this encoding simplify the output logic?

**assign o\_valid = cur\_state[3]; // output is simple!**

How would this encoding impact the next state logic?

**Need to decode 4 bits at a time instead of 3 bits (more gates)**

# Commonly Used Encoding Styles

- Binary (00,01,10,11, ...), most commonly used
- Gray (00,01,11,10, ...), only one bit is changed between two adjacent values
- One-hot (0001, 0010, 0100, 1000), only one bit is “hot” for each state
- Parity (001, 010, 100, 111, ...), parity of all legal states is always 1
- Each encoding style has its own merits, discussion of the merits are however outside of this lecture